



Princess Sumaya  
University  
for Technology

King Abdullah II School of Engineering

EE21221  
Electric Circuits (1)  
Section #4

Quiz #4  
Tuesday 28/12/2021

Name: .....

Q.1) Sketch the voltage which develops across the terminals of a 2.5 F capacitor in response to the current waveforms that is shown in Figure Q.1. [3-Points]


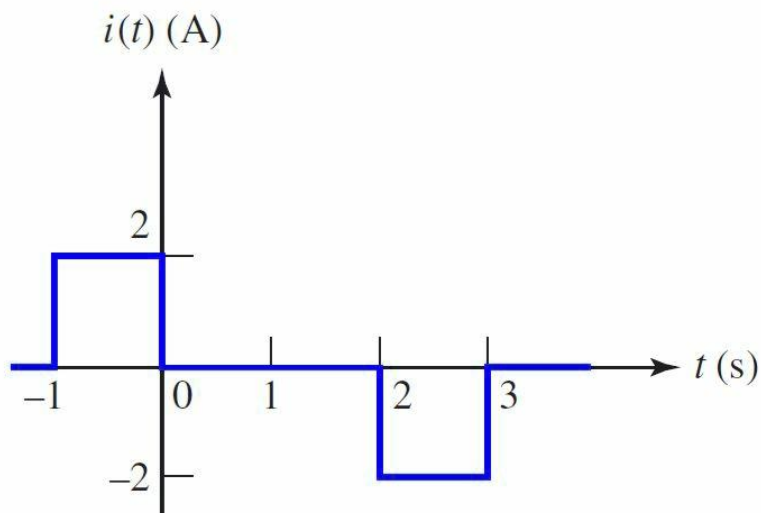
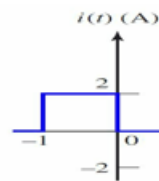


Figure Q.1

Solution:

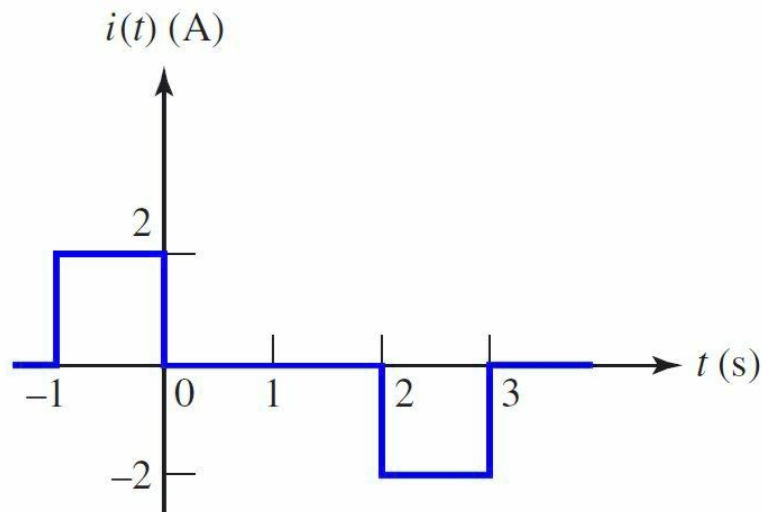

**For  $0 \leq t \leq 2$**

$$v(t) = \frac{1}{2.5} \int_0^t 0 \cdot dt + v(0) = 0.8$$

$$v(t) = 0.8, 0 \leq t \leq 2$$

**For  $-\infty \leq t \leq -1$**

$$i(t) = 0, -\infty \leq t \leq -1$$

$$v(t_0) = v(-\infty) = 0$$

$$v(t) = \frac{1}{2.5} \int_{-\infty}^t 0 \cdot dt + v(-\infty)$$

$$v(t) = 0, -\infty \leq t \leq -1$$

**For  $0 \leq t \leq 2$**

$$v(t) = \frac{1}{2.5} \int_0^t 0 \cdot dt + v(0) = 0.8$$

$$v(t) = 0.8, 0 \leq t \leq 2$$

**For  $2 \leq t \leq 3$**

$$v(t) = \frac{1}{2.5} \int_2^t -2 \cdot dt + v(2)$$

$$= \frac{-2}{2.5} t \Big|_2^t + v(2) = -0.8(t - 2) + v(2)$$

$$v(2) = 0.8$$

$$v(t) = -0.8t + 2.4, 2 \leq t \leq 3$$

**For  $-1 \leq t \leq 0$**

$$i(t) = 2, -1 \leq t \leq 0$$

$$v = \frac{1}{2.5} \int_{-1}^t 2 \cdot dt + v(-1)$$

$$= \frac{2}{2.5} t \Big|_{-1}^t + v(-1)$$

$$= 0.8(t + 1) + v(-1)$$

$$v(-1) = 0$$

$$v(t) = 0.8(t + 1), -1 \leq t \leq 0$$


**For  $t \geq 3$**

$$v(t) = \frac{1}{2.5} \int_3^t 0 \cdot dt + v(3)$$


$$v(3) = 0$$

$$v(t) = 0, t \geq 3$$
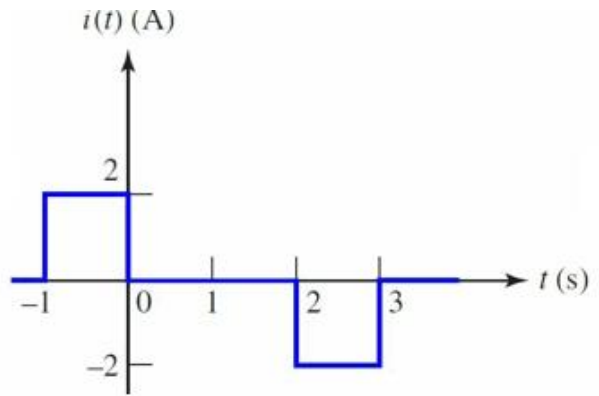
$$\begin{aligned}
 v(t) &= 0, -\infty \leq t \leq -1 \\
 v(t) &= 0.8(t+1), -1 \leq t \leq 0 \\
 v(t) &= -0.8t + 2.4, 2 \leq t \leq 3 \\
 v(t) &= 0, t \geq 3 \\
 v(t) &= 0.8, 0 \leq t \leq 2
 \end{aligned}$$


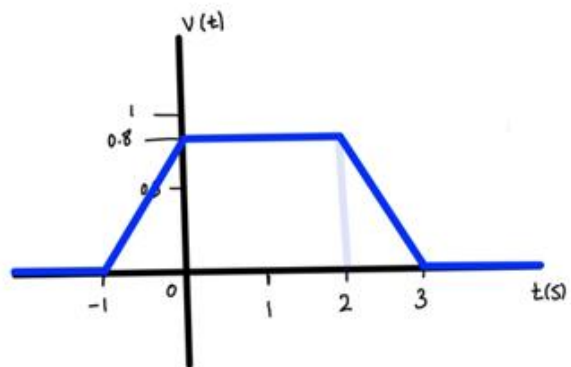
$$V(t) = \begin{cases} 0 & , t \leq -1 \\ 0.8(t+1) & , -1 \leq t \leq 0 \\ 0.8 & , 0 \leq t \leq 2 \\ -0.8t + 2.4 & , 2 \leq t \leq 3 \\ 0 & , t \geq 3 \end{cases}$$



Q.2) Obtain the equivalent resistance  $R_{ab}$  in the circuit shown in Figure Q.2 then use it to find  $i$ . [4-Points]



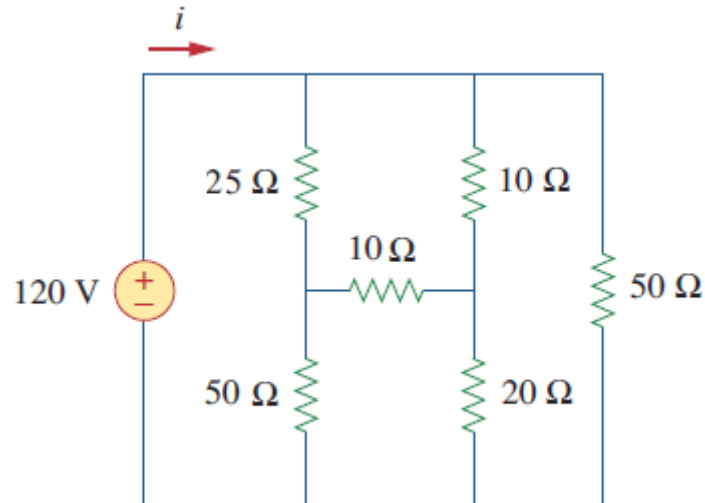


Figure Q.2

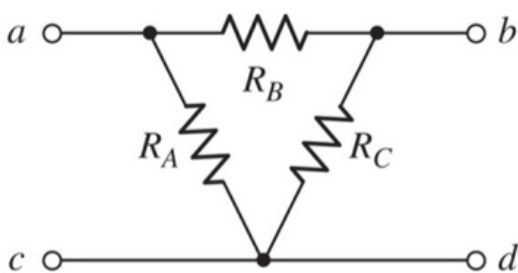

this  $\Delta$  is equivalent to the Y if
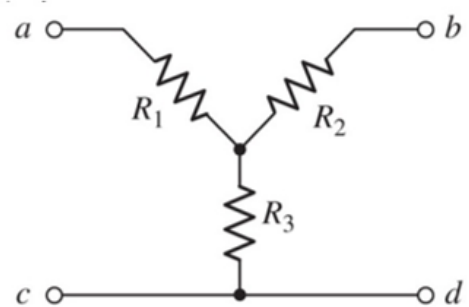
$$\begin{aligned} R_A &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_B &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \\ R_C &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \end{aligned}$$



this Y is equivalent to the  $\Delta$  if

$$\begin{aligned} R_1 &= \frac{R_A R_B}{R_A + R_B + R_C} \\ R_2 &= \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 &= \frac{R_C R_A}{R_A + R_B + R_C} \end{aligned}$$

**Solution:**


$i =$

$R_1=10\ \Omega$ ,  $R_2=20\ \Omega$ , and  $R_3=10\ \Omega$

$$R_a=500/20=25\ \Omega$$

$$R_b=500/10=50\ \Omega$$


$$R_c=500/10=50\ \Omega$$

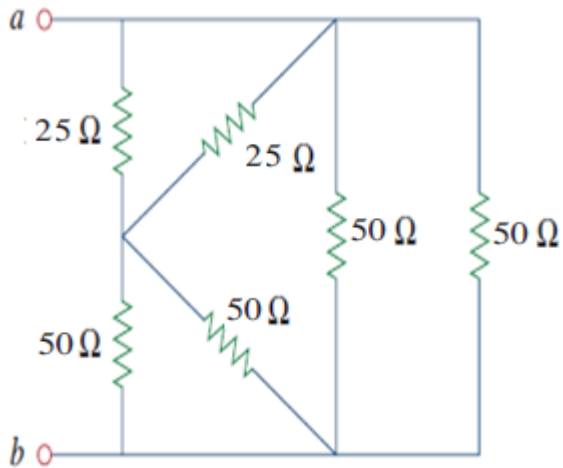

$$50//50=25\ \Omega$$

$$25//25=12.5\ \Omega$$

$$50//50=25\ \Omega$$

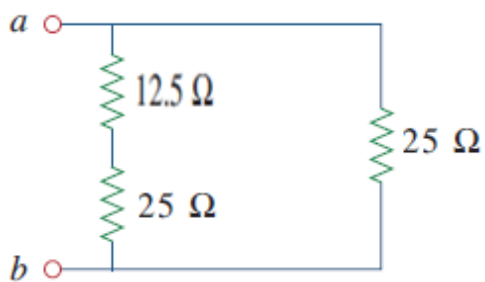


$$12.5+25=37.5\ \Omega$$

$$37.5//25=15\ \Omega$$

$$i=120/15=8\text{A}$$



**Q.3) Obtain the energy stored in the 2 mF capacitor that is shown in Fig. Q.3 under dc conditions. [3-Points]**

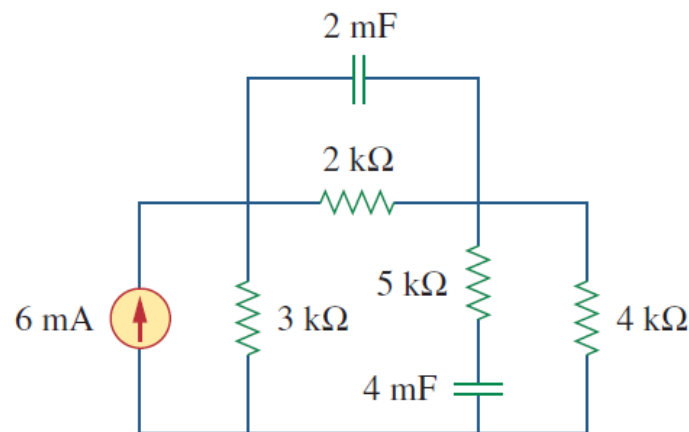

**Figure Q.3**

**Solution:**

$W_{2\text{mF}} =$

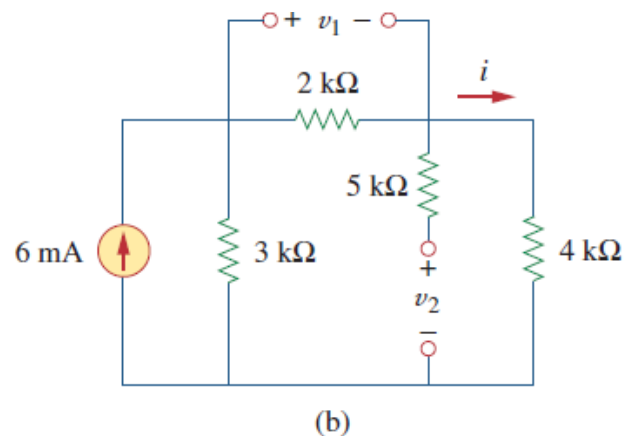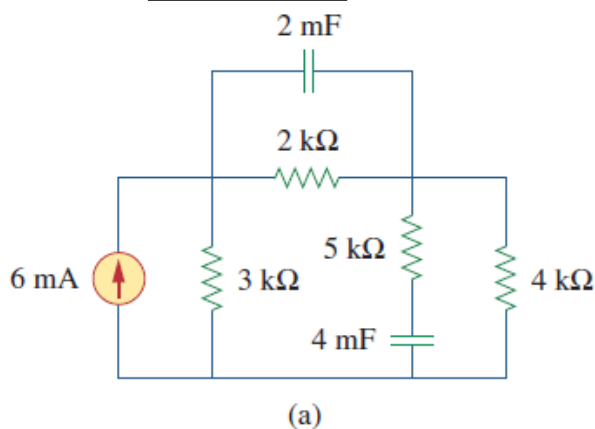

**Solution:**

Under dc conditions, we replace each capacitor with an open circuit, as shown in Fig. 6.12(b). The current through the series combination of the 2-k $\Omega$  and 4-k $\Omega$  resistors is obtained by current division as

$$i = \frac{3}{3 + 2 + 4}(6 \text{ mA}) = 2 \text{ mA}$$

Hence, the voltages  $v_1$  and  $v_2$  across the capacitors are

$$v_1 = 2000i = 4 \text{ V} \quad v_2 = 4000i = 8 \text{ V}$$

and the energies stored in them are

$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(2 \times 10^{-3})(4)^2 = 16 \text{ mJ}$$

$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(4 \times 10^{-3})(8)^2 = 128 \text{ mJ}$$