



Princess Sumaya
University
for Technology

King Abdullah II School of Engineering

EE21221
Electric Circuits (1)
Section #3

Quiz #4
Wednesday 29/12/2021

Name:

Q.1) Sketch the voltage which develops across the terminals of a 2.5 F capacitor in response to the current waveforms that is shown in Figure Q.1. [3-Points]


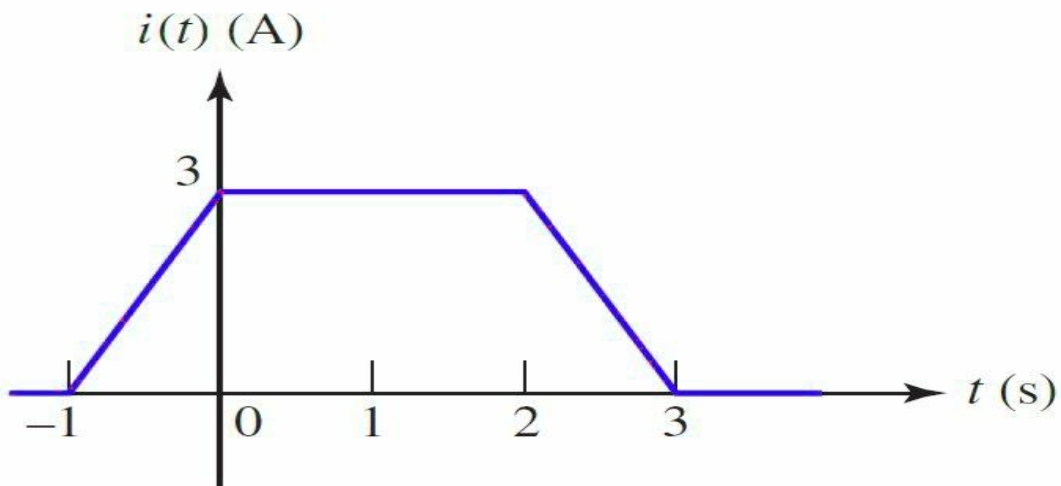
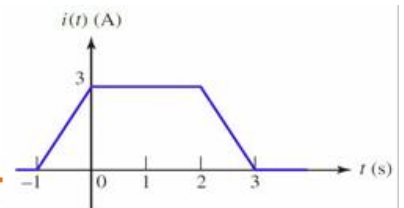


Figure Q.1

Solution:

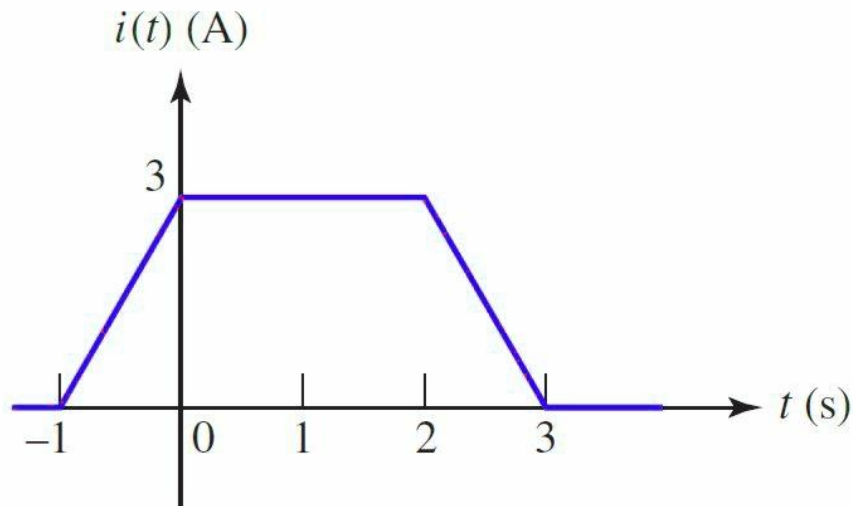

For $-\infty \leq t \leq -1$

$$\begin{aligned}
 i(t) &= 0, -\infty \leq t \leq -1 \\
 v(t_0) &= v(-\infty) = 0 \\
 v(t) &= \frac{1}{2.5} \int_{-\infty}^t 0 \cdot dt + v(-\infty) \\
 v(t) &= 0, -\infty \leq t \leq -1
 \end{aligned}$$

For $-1 \leq t \leq 0$

$$\begin{aligned}
 i(t) &= 3t + 3, -1 \leq t \leq 0 \\
 v &= \frac{1}{2.5} \int_{-1}^t 3t + 3 \cdot dt + v(-1) \\
 &= \frac{1}{2.5} (1.5 t^2 + 3t) \Big|_{-1}^t + v(-1) \\
 v(-1) &= 0 \\
 v &= \frac{1}{2.5} (1.5 t^2 + 3t + 1.5)
 \end{aligned}$$

For $0 \leq t \leq 2$

$$\begin{aligned}
 i(t) &= 3, 0 \leq t \leq 2 \\
 v &= \frac{1}{2.5} \int_0^t 3 \cdot dt + v(0) \\
 &= \frac{3}{2.5} t \Big|_0^t + v(0) \\
 v(0) &= 0.6 \\
 v &= \frac{3}{2.5} t + 0.6 \\
 v(t) &= 1.2t + 0.6, 0 \leq t \leq 2
 \end{aligned}$$

$$v(t) = 0.6 t^2 + 1.2t + 0.6, -1 \leq t \leq 0$$

For $t \geq 3$

$$\begin{aligned}
 v(t) &= \frac{1}{2.5} \int_3^t 0 \cdot dt + v(3) \\
 v(3) &= 3.6 \\
 v(t) &= 3.6, t \geq 3
 \end{aligned}$$

$$v(t) = 0, -\infty \leq t \leq -1$$

$$v(t) = 0.6t^2 + 1.2t + 0.6, -1 \leq t \leq 0$$

$$v(t) = 1.2t + 0.6, 0 \leq t \leq 2$$

$$v(t) = 3.6, t \geq 3$$


For $2 \leq t \leq 3$

$$v(t) = \frac{1}{2.5} \int_2^t 9 - 3t \cdot dt + v(2)$$


$$= \frac{1}{2.5} (9t - 1.5t^2) \Big|_2^t + v(2)$$

$$v(2) = 3$$
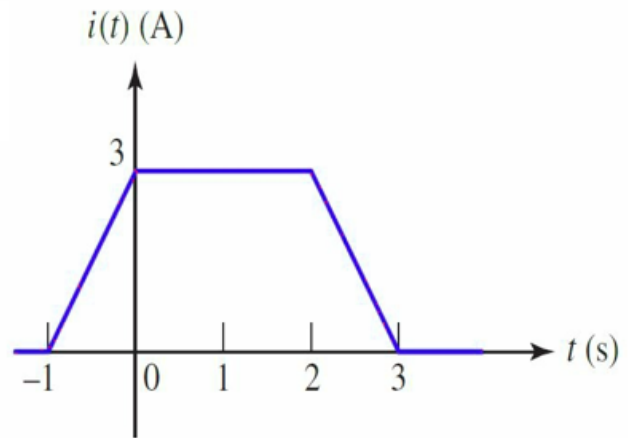
$$v(t) = -0.6t^2 + 3.6t - 1.8, 2 \leq t \leq 3$$


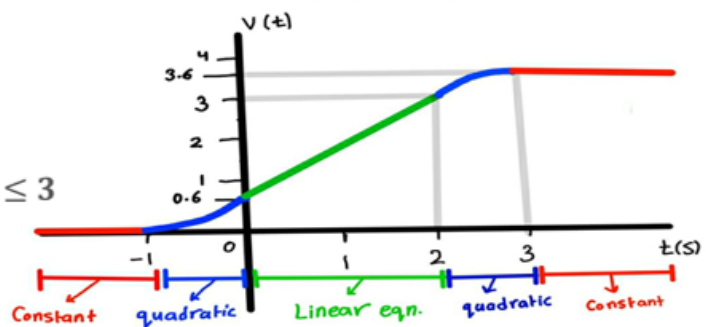
$$v(t) = \begin{cases} 0 & , t \leq -1 \\ 0.6t^2 + 1.2t + 0.6 & , -1 \leq t \leq 0 \\ 1.2t + 0.6 & , 0 \leq t \leq 2 \\ -0.6t^2 + 3.6t - 1.8 & , 2 \leq t \leq 3 \\ 3.6 & , t \geq 3 \end{cases}$$



Q.2) Obtain the equivalent resistance R_{ab} in the circuit shown in Figure Q.2 then use it to find i . [4-Points]



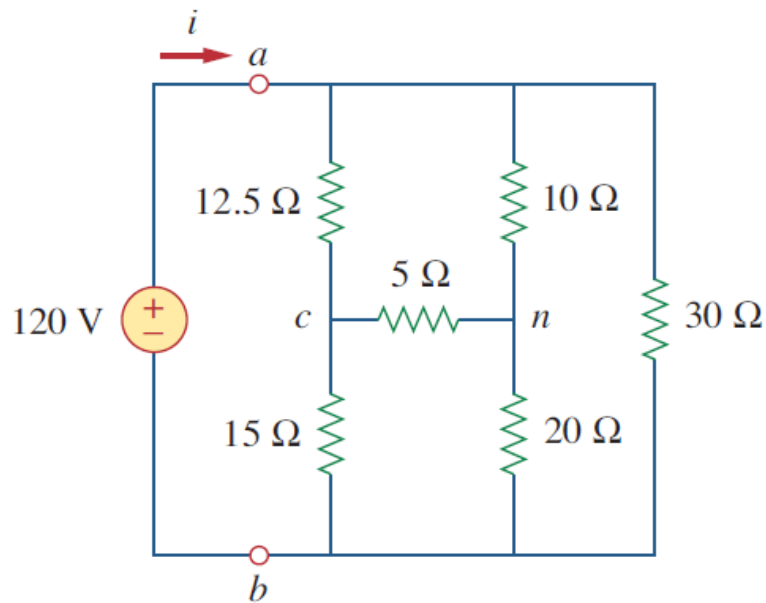


Figure Q.2

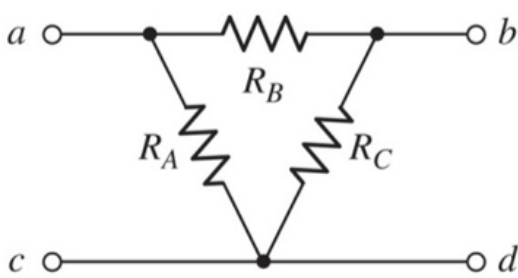

this Δ is equivalent to the Y if
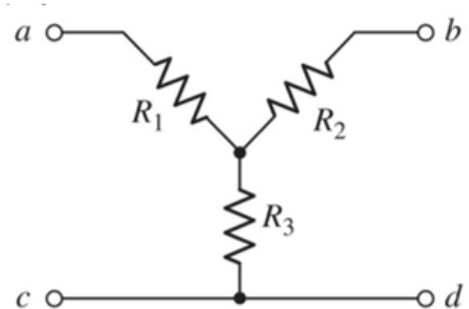
$$\begin{aligned} R_A &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_B &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \\ R_C &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \end{aligned}$$



this Y is equivalent to the Δ if

$$\begin{aligned} R_1 &= \frac{R_A R_B}{R_A + R_B + R_C} \\ R_2 &= \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 &= \frac{R_C R_A}{R_A + R_B + R_C} \end{aligned}$$

Solution:

$i =$

Two Methods:

First one:

$$R_1 = 10 \, \Omega, \quad R_2 = 20 \, \Omega, \quad R_3 = 5 \, \Omega$$


Thus from Eqs. (2.53) to (2.55) we have

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10}$$

$$= \frac{350}{10} = 35 \, \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5 \, \Omega$$
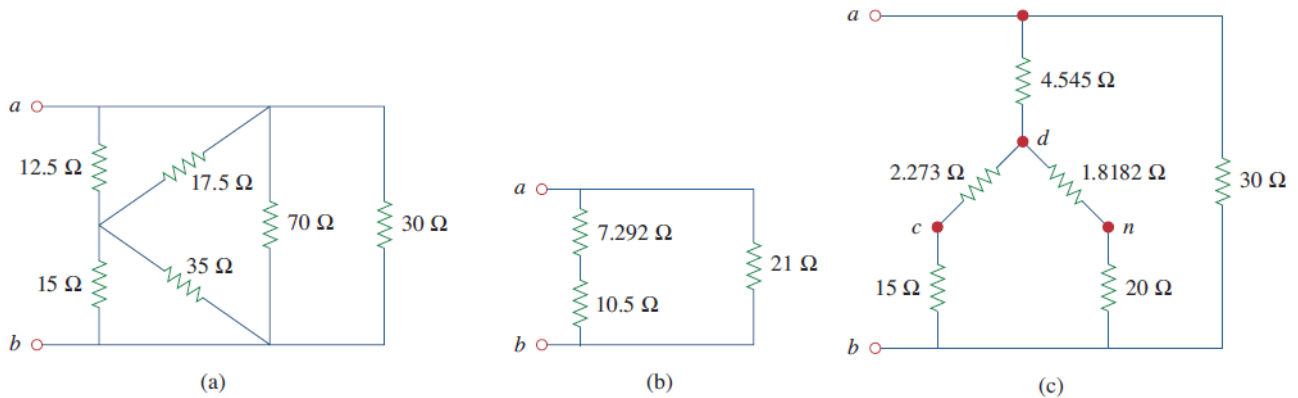
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70 \, \Omega$$



With the Y converted to Δ , the equivalent circuit (with the voltage source removed for now) is shown in Fig. 2.53(a). Combining the three pairs of resistors in parallel, we obtain

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \, \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.292 \, \Omega$$

$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \, \Omega$$

so that the equivalent circuit is shown in Fig. 2.53(b). Hence, we find

$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = \mathbf{9.632 \, \Omega}$$

Then

$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = \mathbf{12.458 \, A}$$

Second Method:

Evaluate. Now we must determine if the answer is correct and then evaluate the final solution.

It is relatively easy to check the answer; we do this by solving the problem starting with a delta-wye transformation. Let us transform the delta, *can*, into a wye.

Let $R_c = 10\ \Omega$, $R_a = 5\ \Omega$, and $R_n = 12.5\ \Omega$. This will lead to (let d represent the middle of the wye):

$$R_{ad} = \frac{R_c R_n}{R_a + R_c + R_n} = \frac{10 \times 12.5}{5 + 10 + 12.5} = 4.545\ \Omega$$

$$R_{cd} = \frac{R_a R_n}{27.5} = \frac{5 \times 12.5}{27.5} = 2.273\ \Omega$$

$$R_{nd} = \frac{R_a R_c}{27.5} = \frac{5 \times 10}{27.5} = 1.8182\ \Omega$$

This now leads to the circuit shown in Figure 2.53(c). Looking at the resistance between d and b , we have two series combination in parallel, giving us

$$R_{db} = \frac{(2.273 + 15)(1.8182 + 20)}{2.273 + 15 + 1.8182 + 20} = \frac{376.9}{39.09} = 9.642\ \Omega$$

This is in series with the $4.545\text{-}\Omega$ resistor, both of which are in parallel with the $30\text{-}\Omega$ resistor. This then gives us the equivalent resistance of the circuit.

$$R_{ab} = \frac{(9.642 + 4.545)30}{9.642 + 4.545 + 30} = \frac{425.6}{44.19} = \mathbf{9.631\ \Omega}$$

This now leads to

$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.631} = \mathbf{12.46\ A}$$

We note that using two variations on the wye-delta transformation leads to the same results. This represents a very good check.

Q.3) Obtain the energy stored in the 4 mF capacitor that is shown in Fig. Q.3 under dc conditions. [3-Points]

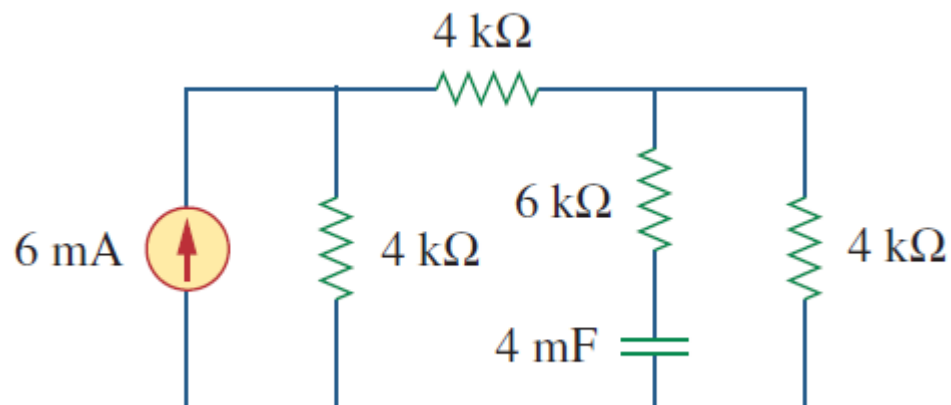


Figure Q.3

Solution:

$W_{4\text{mF}} =$

$$i_{4k} = (6\text{mA} \cdot 4\text{K}) / 12\text{K} = 2\text{mA}$$

$$V_c = 2\text{mA} \cdot 4\text{K} = 8\text{V}$$

$$W = 0.5 C V^2 = 0.5 \cdot 4\text{m} \cdot 8 \cdot 8 = 0.128 \text{ J}$$